

# Laboratory Exercise 5

## Timers and Real-time Clock

The purpose of this exercise is to study the use of clocks in timed circuits. The designed circuits are to be implemented on an Altera DE1 board.

### Background

In VHDL language we can describe a variable-size counter by using a *generic* declaration. An example of an  $n$ -bit counter is shown in Figure 1.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_signed.all;

entity counter is
  generic (
    n : natural := 4;
  );
  port (
    clock : in STD_LOGIC;
    reset_n : in STD_LOGIC;
    Q : out STD_LOGIC_VECTOR(n-1 downto 0)
  );
end entity;

architecture rtl of counter is
  signal value : std_logic_vector(n-1 downto 0);
begin
  PROCESS(clock, reset_n)
  begin
    if (reset_n = '0') then
      value <= (OTHERS => '0');
    elsif ((clock'event) and (clock = '1')) then
      value <= value + 1;
    end if;
  end process;
  Q <= value;
end rtl;
```

Figure 1: A VHDL description of an  $n$ -bit counter.

The parameter  $n$  specifies the number of bits in the counter. A particular value of this parameter is defined by using a **generic map** statement. For example, an 8-bit counter can be specified as:

```

eight_bit: counter
  generic map( n => 8 )
  port map eight_bit(clock, reset_n, Q);

```

By using parameters we can instantiate counters of different sizes in a logic circuit, without having to create a new module for each counter.

## Part I

Create a modulo- $k$  counter by modifying the design of an 8-bit counter to contain an additional parameter. The counter should count from 0 to  $k - 1$ . When the counter reaches the value  $k - 1$  the value that follows should be 0.

Your circuit should use pushbutton  $KEY_0$  as an asynchronous reset,  $KEY_1$  as a manual clock input. The contents of the counter should be displayed on red LEDs. Compile your design with Quartus II software, download your design onto a DE1 board, and test its operation. Perform the following steps:

1. Create a new Quartus II project which will be used to implement the desired circuit on the DE1 board.
2. Write a VHDL file that specifies the desired circuit.
3. Include the VHDL file in your project and compile the circuit.
4. Simulate the designed circuit to verify its functionality.
5. Assign the pins on the FPGA to connect to the lights and pushbutton switches, by importing the pin-assignment file *DE1\_pin\_assignments.qsf*.
6. Recompile the circuit and download it into the FPGA chip.
7. Verify that your circuit works correctly by observing the display.

## Part II

Implement a 3-digit BCD counter. Display the contents of the counter on the 7-segment displays,  $HEX2-0$ . Derive a control signal, from the 50-MHz clock signal provided on the DE1 board, to increment the contents of the counter at one-second intervals. Use the pushbutton switch  $KEY_0$  to reset the counter to 0.

## Part III

Design and implement a circuit on the DE1 board that acts as a real-time clock. It should display the minutes (from 0 to 60) on  $HEX3-2$  and the seconds (from 0 to 60) on  $HEX1-0$ . Use the switches  $SW_{7-0}$  to preset the minute part of the time displayed by the clock.

## Part IV

An early method of telegraph communication was based on the Morse code. This code uses patterns of short and long pulses to represent a message. Each letter is represented as a sequence of dots (a short pulse), and dashes (a long pulse). For example, the first eight letters of the alphabet have the following representation:

A	• —
B	— • • •
C	— • — •
D	— • •
E	•
F	• • — •
G	— — •
H	• • • •

Design and implement a circuit that takes as input one of the first eight letters of the alphabet and displays the Morse code for it on a red LED. Your circuit should use switches  $SW_{2-0}$  and pushbuttons  $KEY_{1-0}$  as inputs. When a user presses  $KEY_1$ , the circuit should display the Morse code for a letter specified by  $SW_{2-0}$  (000 for A, 001 for B, etc.), using 0.5-second pulses to represent dots, and 1.5-second pulses to represent dashes. Pushbutton  $KEY_0$  should function as an asynchronous reset. A high-level schematic diagram of the circuit is shown in Figure 2.

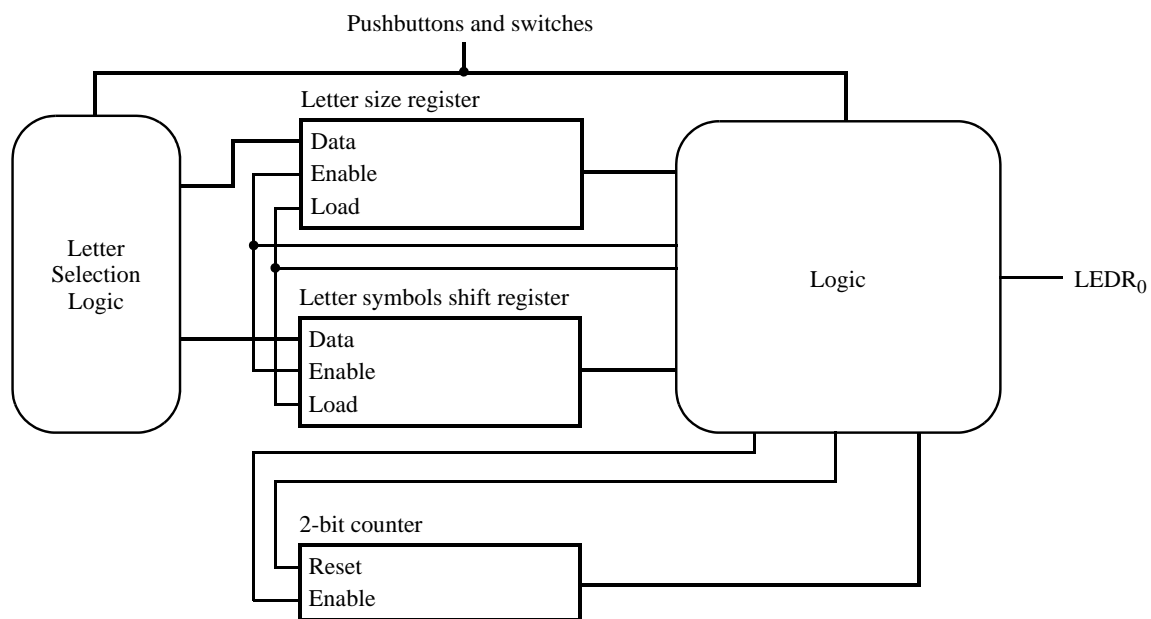


Figure 2: High-level schematic diagram of the circuit for part IV.

**Hint:** Use a counter to generate 0.5-second pulses, and another counter to keep the  $LED R_0$  light on for either 0.5 or 1.5 seconds.

## **Preparation**

The recommended preparation for this laboratory exercise includes:

1. VHDL code for **Part I**
2. Simulation of the VHDL code for **Part I**
3. VHDL code for **Part II**
4. VHDL code for **Part III**

Copyright ©2011 Altera Corporation.